

Name:	Nandana P
Register No.:	727721EUEC096
Subject Code and Subject Title:	21EC504- VLSI Design
Internal Component:	Simulation using EDA Playground
Date:	11 th October, 2023

1. Simulate the following gates and combinational circuits using EDA Playground:

- i) XOR
- ii) XNOR
- iii) 8 x 1 MUX
- iv) 5 input NAND

a) XOR

Testbench code:

```

module myxor_tb;
    reg a1,b1;
    wire y1;

    myxor myxor_tb(.a(a1),.b(b1),.y(y1));
    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);

        // $monitor(a1,b1,y1);
        a1=1'b0;
        b1=1'b0;
        #1 $display("a1:%b, b1:%b, y1:%b",a1,b1,y1);
        #1
        a1=1'b0;
        b1=1'b1;
        #1 $display("a1:%b, b1:%b, y1:%b",a1,b1,y1);
        #1
        a1=1'b1;
        b1=1'b0;

```

```

    #1 $display("a1:%b, b1:%b, y1:%b",a1,b1,y1);

#1

a1=1'b1;
b1=1'b1;

    #1 $display("a1:%b, b1:%b, y1:%b",a1,b1,y1);
end

endmodule

```

VHDL code:

```

module myxor (a,b,y);

    input a,b;

    output y;


    assign y = a^b; //dataflow


endmodule

```

Simulation:

Log Share

 [2023-09-24 13:40:54 UTC] iverilog '-wall' design.sv testbench.sv && unbuffer vvp a.out
VCD info: dumpfile dump.vcd opened for output.
a1:0, b1:0, y1:0
a1:0, b1:1, y1:1
a1:1, b1:0, y1:1
a1:1, b1:1, y1:0
Finding VCD file...
./dump.vcd



b) XNOR

Testbench code:

```
module XNOR_Gate_tb;

    reg A;
    reg B;
    wire Y;
    integer i;

    XNOR_Gate inst(.A(A), .B(B), .Y(Y));

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars;
        #100 $finish;
    end


    initial
    begin
        A <= 0;
        B <= 0;
        $monitor ("A=%0b B=%0b Y=%0b", A, B, Y);
        for (i=0; i< 4; i= i + 1)
        begin
            {A, B} = i;
            #10;
        end
    end
endmodule
```

Verilog code:

```
module XNOR_Gate(
    input A,
    input B,
    output Y);
    assign Y = ~ (~A&&B || A&&~B);
endmodule
```

Simulation:
 
```
Log Share
[2023-09-24 16:46:44 UTC] iverilog '-wall' design.sv testbench.sv && unbuffer vvp a.out
VCD info: dumpfile dump.vcd opened for output.
A=0 B=0 Y=1
A=0 B=1 Y=0
A=1 B=0 Y=0
A=1 B=1 Y=1
Done
```



c) 8 x 1 Multiplexer

Testbench code:

-- Testbench for 8 to 1 Multiplexer

entity testbench is

-- empty

end testbench;

architecture tb of testbench is

-- DUT component

component mux8to1 is

port

(s : in bit_vector (2 downto 0);

d : in bit_vector (7 downto 0);

y : out bit);

end component;

signal s : bit_vector (2 downto 0);

signal d : bit_vector (7 downto 0);

signal y : bit;

begin

-- Connect DUT

DUT: mux8to1 port map(

```

s => s,
d => d,
y => y );
process
begin
  s <= "000";
  d <= "00000001";
  wait for 1 ns;
  s <= "001";
  d <= "00000010";
  wait for 1 ns;
  s <= "010";
  d <= "00000100";
  wait for 1 ns;
  s <= "011";
  d <= "00001000";
  wait for 1 ns;
  s <= "100";
  d <= "00010000";
  wait for 1 ns;
  s <= "101";
  d <= "00100000";
  wait for 1 ns;
  s <= "110";
  d <= "01000000";
  wait for 1 ns;
  s <= "111";
  d <= "10000000";
  wait for 1 ns;
  wait;
end process;
end tb;

```

Verilog code:

-- Simple 8 to 1 Multiplexer design

```
entity mux8to1 is
port ( s : in bit_vector (2 downto 0);
      d : in bit_vector (7 downto 0);
      y : out bit);
end mux8to1;
```

architecture equation of mux8to1 is

begin

with s select

y <= d(0) when "000",

d(1) when "001",

d(2) when "010",

d(3) when "011",

d(4) when "100",


d(5) when "101",

d(6) when "110",

d(7) when others;

end equation;

Simulation:

 

d) 5 INPUT NAND

Testbench code:

```
module testbench;
```

```
reg A, B, C, D, E;
```

```
wire Y;
```

```
// Instantiate the 5-Input NAND gate
```

```

nand5 uut (
    .A(A),
    .B(B),
    .C(C),
    .D(D),
    .E(E),
    .Y(Y)
);

// Add $dumpfile and $dumpvars
initial begin
    $dumpfile("dump.vcd"); // Specify the VCD file name
    $dumpvars; // Dump all the signals

    $display("A\tB\tC\tD\tE\t\tY");
    $display("-----|---");

    A = 0; B = 0; C = 0; D = 0; E = 0;
    #10; // Wait for a moment
    A = 1; B = 0; C = 1; D = 0; E = 1;
    #10; // Wait for a moment
    A = 1; B = 1; C = 1; D = 1; E = 1;
    #10; // Wait for a moment
    $finish; // End the simulation
end

endmodule

```

Verilog code:

```

// Code your design here

module nand5 (
    input A,
    input B,
    input C,
    input D,
    input E,
    output Y
);

    assign Y = ~(A & B & C & D & E);

endmodule

```

Simulation:

